

---

# Memory Design

張孟洲

國立彰化師範大學電子系教授

---

# Outline

---

- **Memory Classification**
  - Memory cells
    - Static memory cell
    - Dynamic memory cell
    - ROM cells
  - Address decoders
-

# Classification of Memories

---

RWMemory		NVRWM	ROM
Random Access	Non-Random Access	EPROM EEPROM	Mask Programmed
<b>SRAM (Static)</b> <b>DRAM (Dynamic)</b>	FIFO (Queue) LIFO (Stack) SR (Shift Register) <b>CAM (Content Addressable)</b>	<b>FLASH</b>	PROM (Fuse Programmed)

---



# Memory Design (cont.)

---

- Static vs. dynamic RAM
  - Dynamic needs refreshing
    - Refreshing: read, then write back to restore charge
    - Either periodically or after each read
- Static (SRAM)
  - Data stored as long as supply voltage is applied
  - Large (6 transistors/cell)
  - Fast
- Dynamic (DRAM)
  - Periodic refresh required
  - Small (1-3 transistors/cell)
  - Slower
  - Special fabrication process

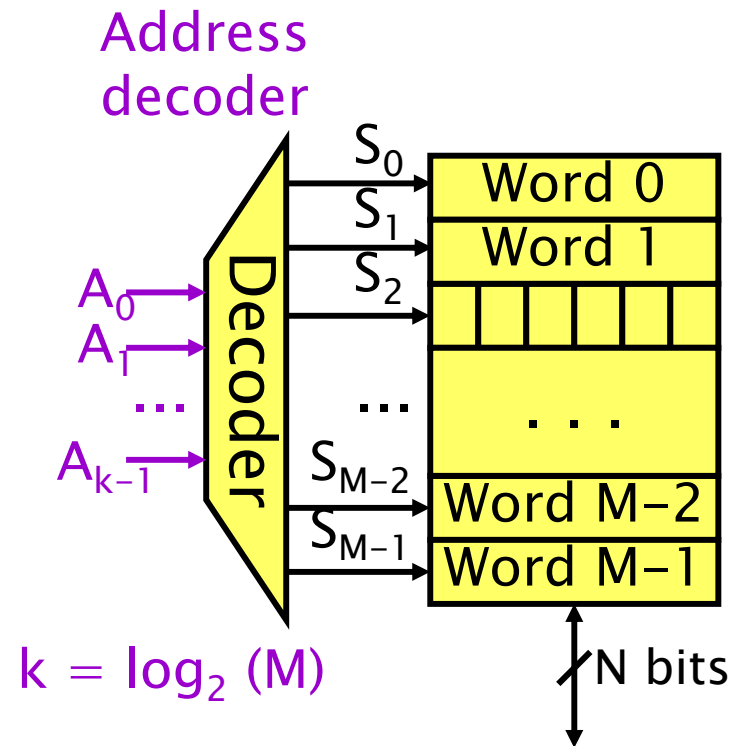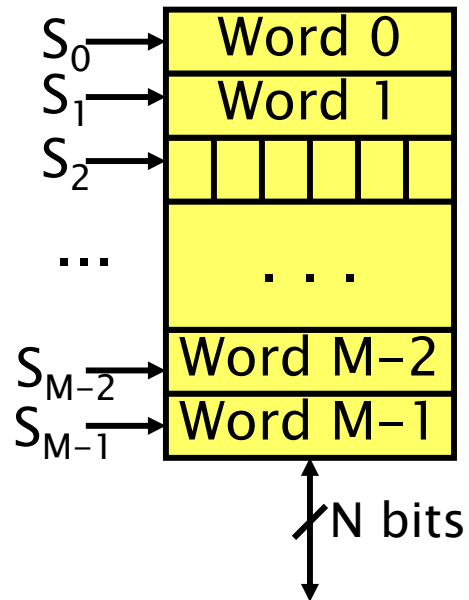
# Memory Architecture: the Big Picture

- Address: which one of the M words to access
- Data: the N bits of the word are read/written


 
# Memory Access Timing: the Big Picture

- Timing:
  - Send address on the address lines, wait for the word line to become stable
  - Read/write data on the data lines




# Outline

---

- Registers (flip-flops), shift registers
  - Memory interface
  - Memory cells
    - **Static memory cell**
    - Dynamic memory cell
    - ROM cells
  - Address decoders
  - Content addressable memory (CAM)
  - Non volatile memory cells
-
 
# Memory Cell: Static RAM (8 transistors)


- 8-transistor cell
  - Bit<sub>i</sub> is the data bus
  - S<sub>j</sub> is the word line
  - Bit' used to reduce delay
- Bus drivers
  - Sense Amplifier (inverter with high gain) used for fast switching
  - Make sure inverters in cell are weaker than the combination of “write buffer” and pass transistor






 
# Memory Cell: Static RAM (6 transistors)

- 6-transistor cell
  - Must adjust inverters for input coming through n-type pass gate
- Bus drivers
  - Must adjust **senseAmp** for input coming through n-type pass gate
  - Harder to drive 1 than 0 through **write buffer** (high resistance via n-transistor)
  - One side is sending 0 anyway (bit or bit') → written correctly



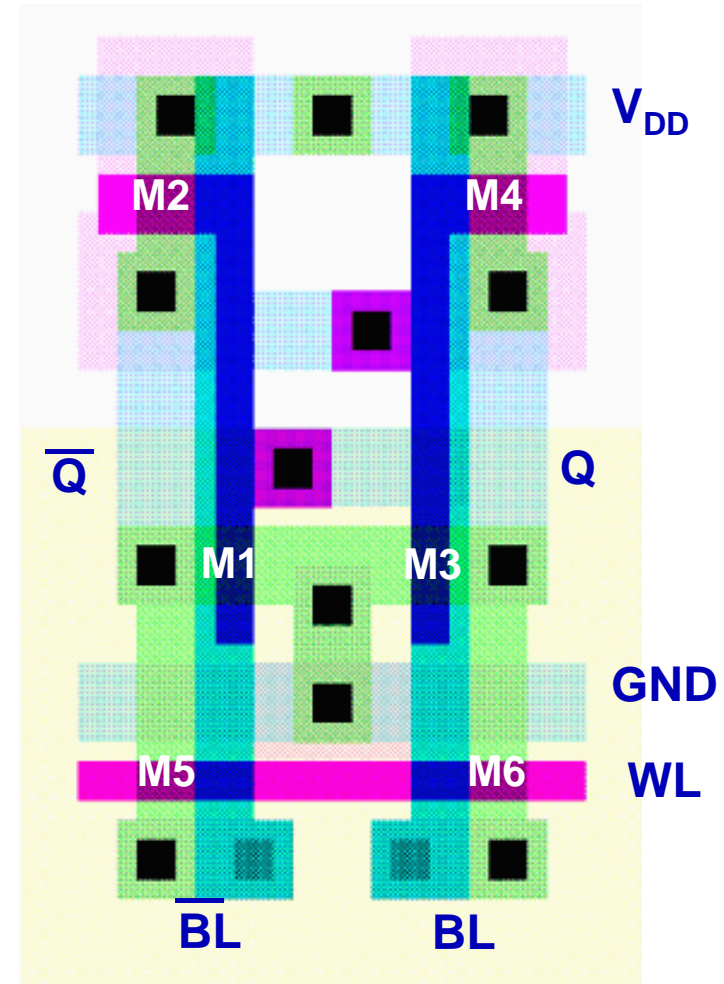 
# 6-Transistor SRAM Cell: Layout

- WL is word line (select line  $S_j$ )
- BL is bit line (bit<sub>*i*</sub>)


 
# 6-Transistor Memory Array

- 8 words deep RAM, 2 bits wide words
- To write to word  $j$ :
  - Set  $S_j=1$ , all other  $S$  lines to 0
  - Send data on the global  $\text{bit}_0, \text{bit}_0', \text{bit}_1, \text{bit}_1'$
- To read word  $k$ :
  - Set  $S_k=1$ , all other  $S$  lines to 0
  - Sense data on  $\text{bit}_0$  and  $\text{bit}_1$ .




# Outline

---

- Memory interface
  - Memory cells
    - Static memory cell
    - **Dynamic memory cell**
    - ROM cells
  - Address decoders
-

 
# Dynamic RAM 4-Transistor Cell

- 4-transistor cell
- Dynamic charge storage must be refreshed
- Dedicated busses for reading and writing



 
# Dynamic RAM 3-Transistor Cell

- 3-transistor cell
  - No p-type transistors yield a very compact layout for cell
  - No V<sub>dd</sub> connection
  - Sense Amplifier must be able to quickly detect dropping voltage
- Precharge data\_out' to generate '1' outputs



# Dynamic RAM 3-Transistor Cell: Timing


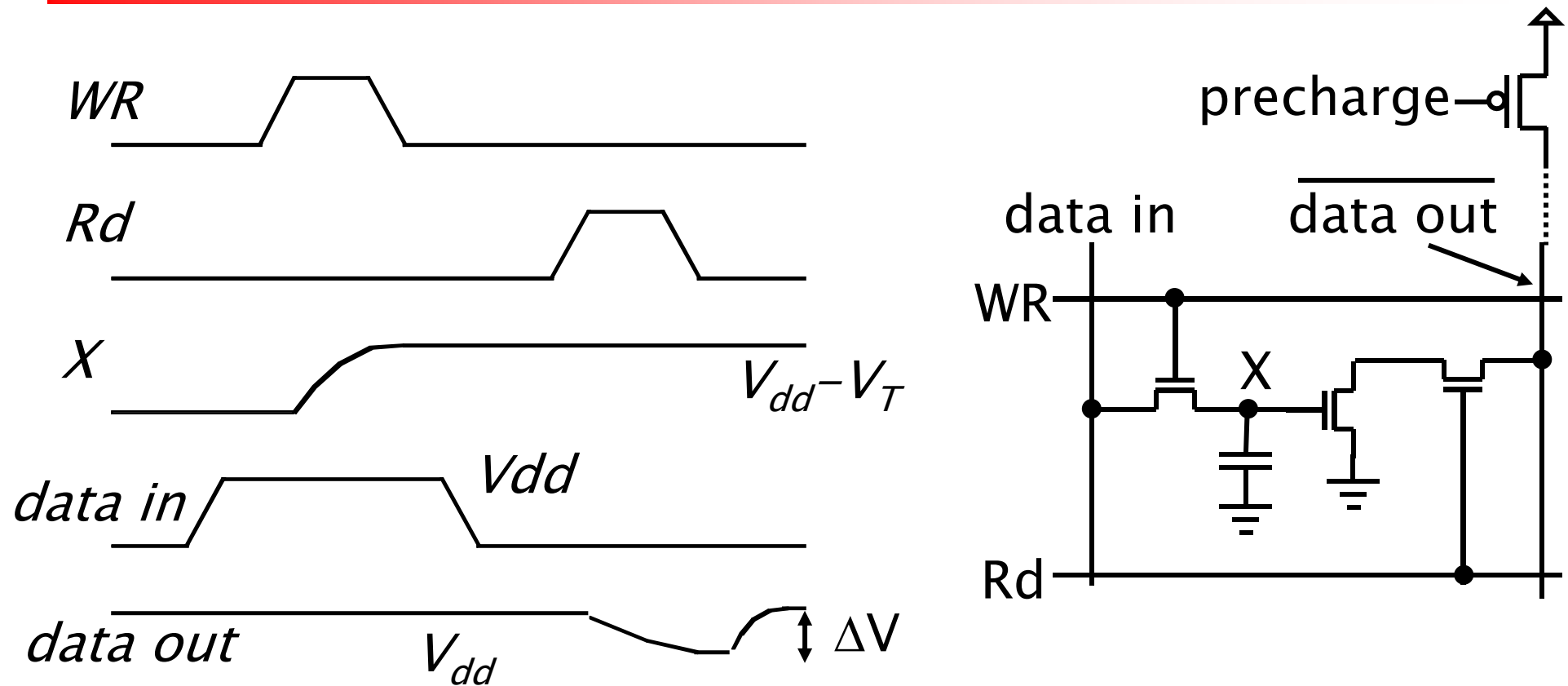


Value stored at node X when writing a "1" =  $V_{WR} - V_{Tn}$

[Rab96] p.586

[©Prentice Hall]


# Dynamic RAM 3-Transistor Cell: Layout

  




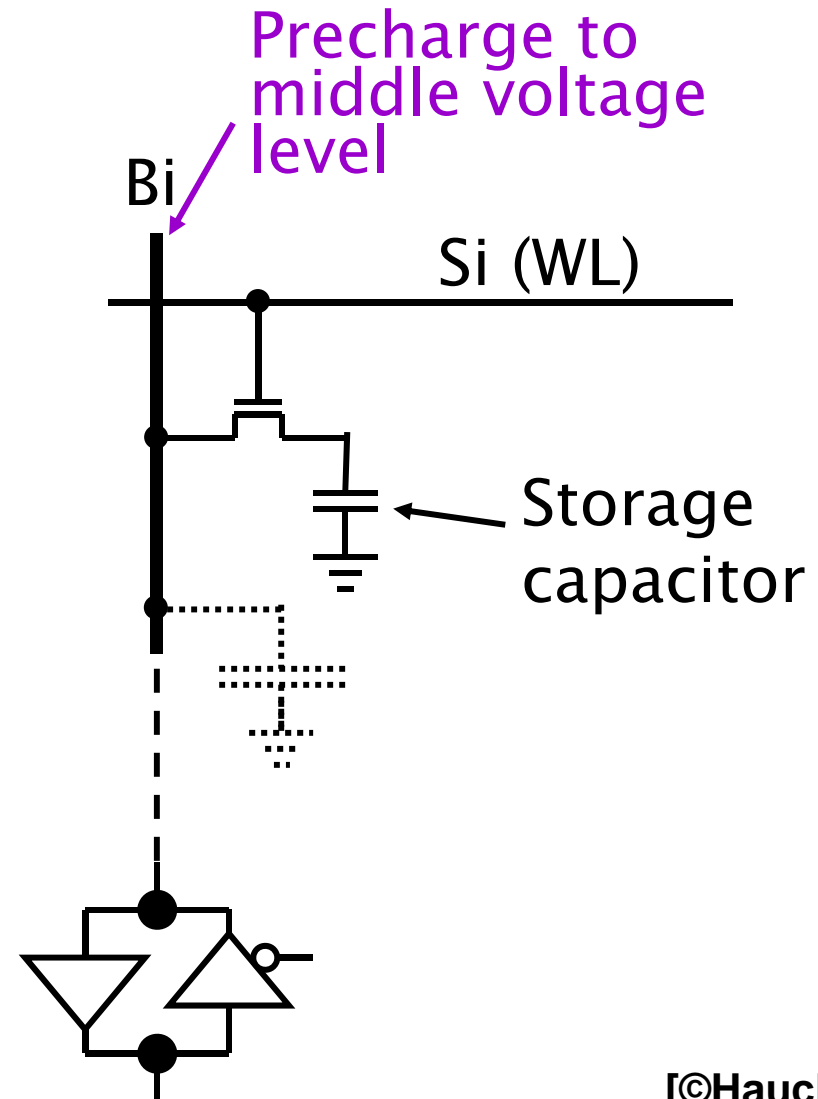
# Dynamic RAM 1-Transistor Cell

- 1-transistor cell
  - Storage capacitor is source of cell transistor
  - Special processing steps to make the storage capacitor large
  - Charge sharing with bus capacitance ( $C_{\text{cell}} \ll C_{\text{bus}}$ )
  - Extra demand on sense amplifier to detect small changes
  - Destructive read (must write immediately)



# Dynamic RAM 1-Transistor Cell: Timing

 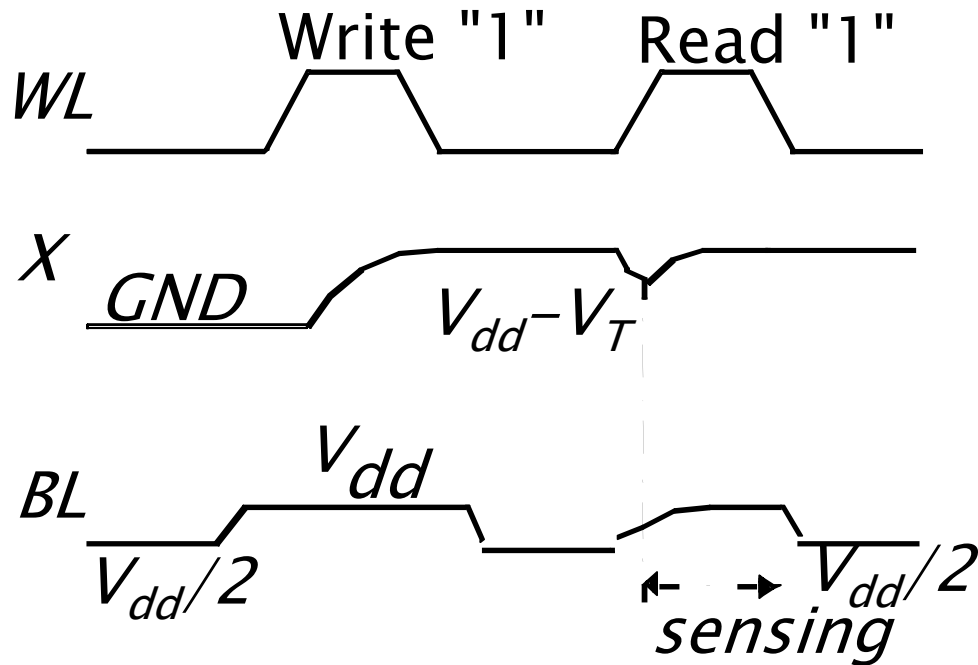

- Write:  $C_s$  is charged/discharged
- Read
  - Voltage swing is small ( $\sim 250$  mV)

- $$\Delta V = V_{BL} - V_{PRE} = (V_X - V_{PRE}) \cdot C_S / (C_S + C_{BL})$$


[Rab96] p.587  
[©Prentice Hall]

# Dynamic RAM 1-Transistor Cell: Observations

---

- DRAM memory cell is single-ended
- Read operation is destructive
- Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design
  - Polysilicon-diffusion plate capacitor
  - Trench or stacked capacitor
- When writing a "1" into a DRAM cell, a threshold voltage is lost
  - Set WL to a higher value than Vdd

# Dynamic RAM 1-Transistor Cell: Layout

 

(a) Cross-section


(b) Layout

Used Polysilicon-Diffusion Capacitance


**Expensive in Area**

# Dynamic RAM 1-Transistor Cell: Layout



---

 

# Dynamic RAM 1-Transistor Cell: Layout

 

Trench Cell

  


Stacked-capacitor Cell

# RAM Cells: Summary

---

- **Static**
  - Fastest (no refresh)
  - Simple design
  - Right solution for small memory arrays such as register files
- **Dynamic**
  - Densest: 1T is best and is the way to go for large memory arrays
  - Built-in circuitry to step through cells and refresh (can do more than one word at a time)
  - Sense amplifier needed for fast read operation

# Multi-Port RAM Cells

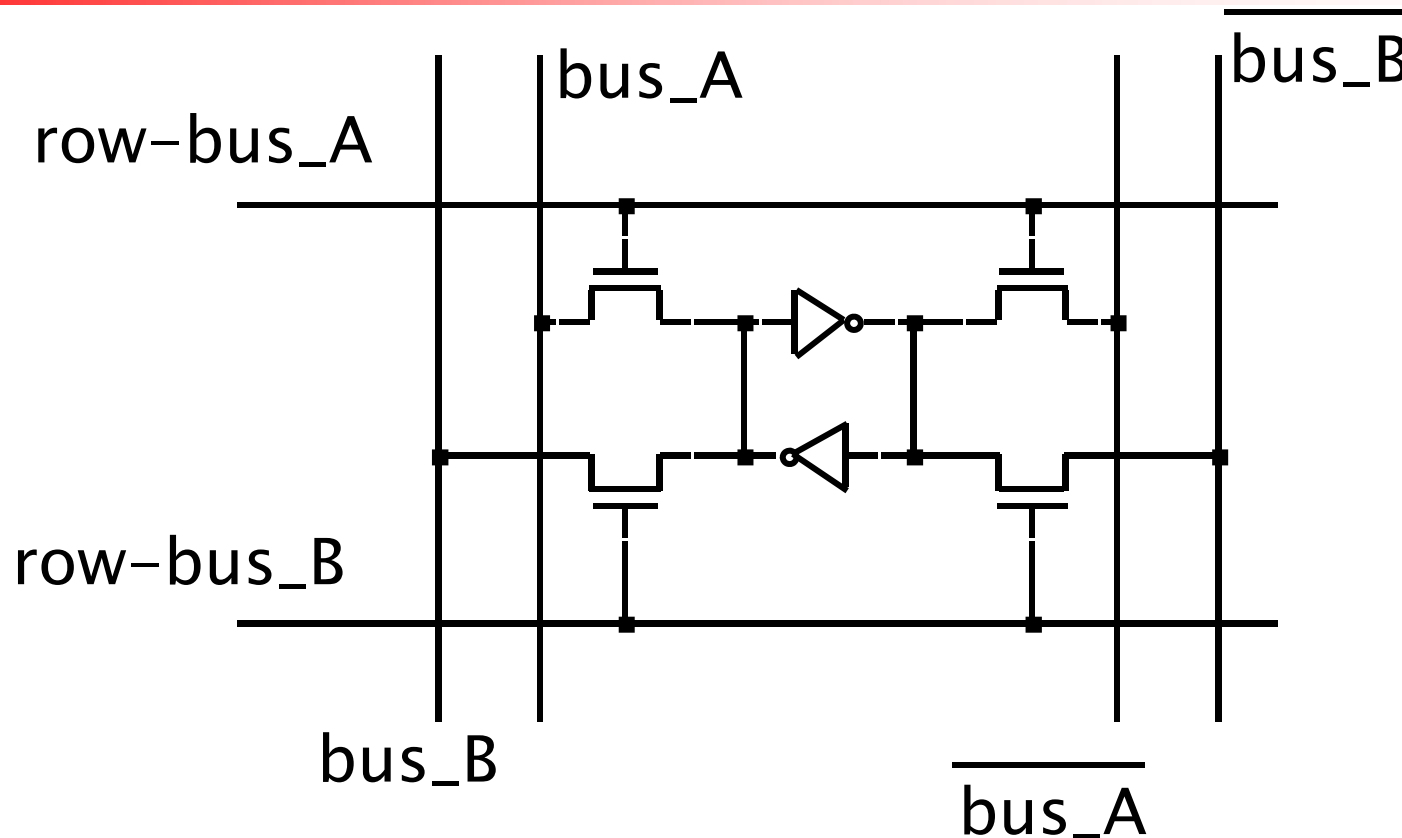


- Idea: add more input and output transistors
- Can be applied to all variants
  - Usually not done for 1T cells


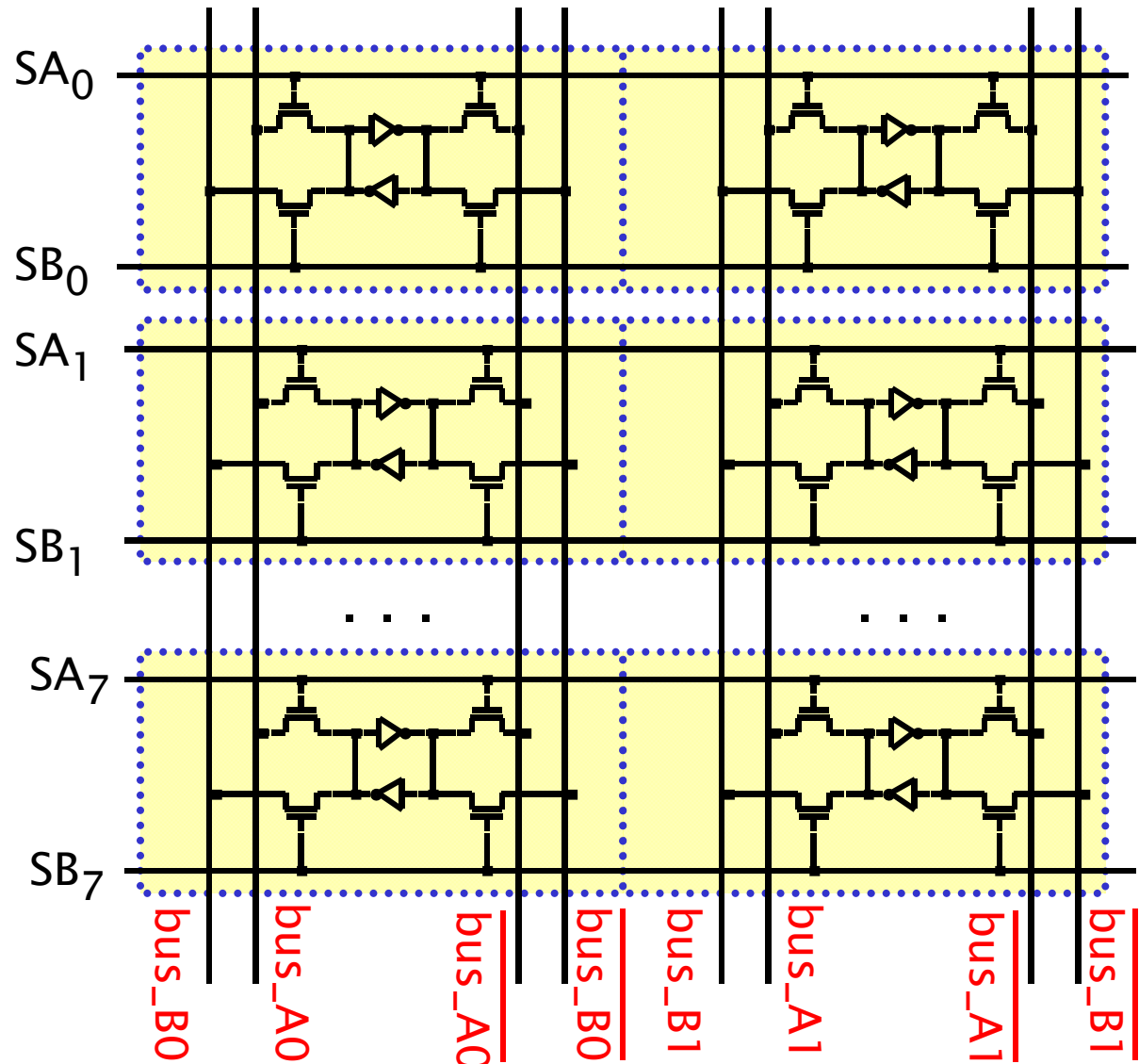
# Multi-Port RAM Cells Array

- 7 words deep, 2 wide words, dual port mem
- To read from word  $j$  and write " $d_1d_0$ " to word  $k$  simultaneously:
  - Set  $SA_j=1$ , and all other  $SA$ 's=0
  - Set  $SB_k=1$ , and all other  $SB$ 's=0
  - Sense the values on  $bus\_A0$  and  $bus\_A1$
  - Write  $d_1d_0$  to  $bus\_B0$  and  $bus\_B1$




# Outline

---


- Memory interface
  - Memory cells
    - Static memory cell
    - Dynamic memory cell
    - **ROM cells**
  - Address decoders
-
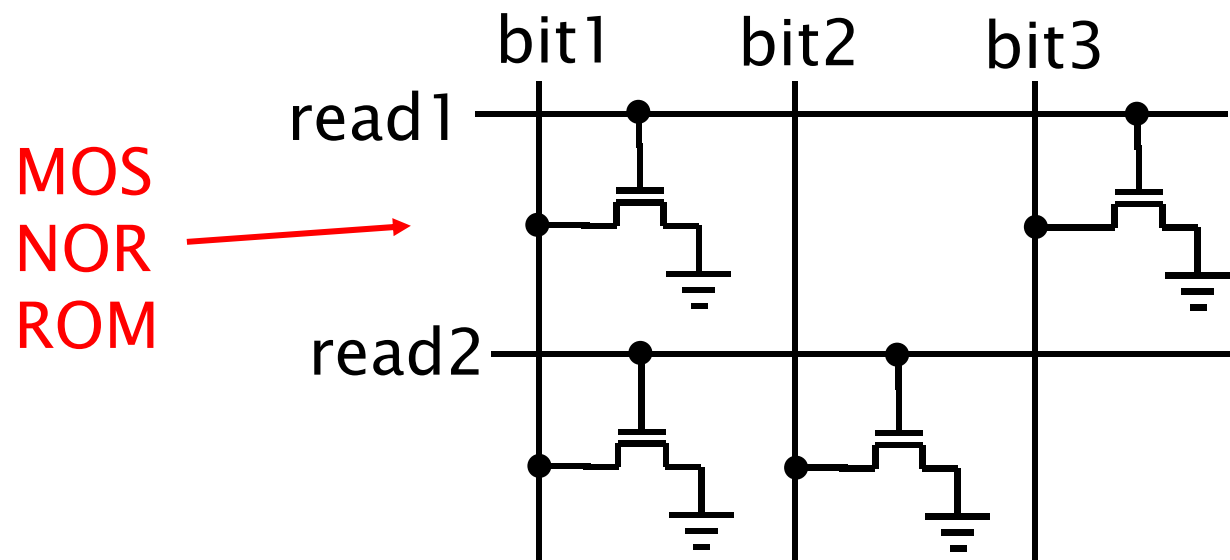
# Read Only Memory (ROM) Cells: MOS NOR

- To store constants data or invariant code
- Popular for control implementation
  - Store program or state machine
- Programmable logic array structure
- Can be **precharged** or **pseudo-nMos**




# ROM Cell: MOS NOR Layout

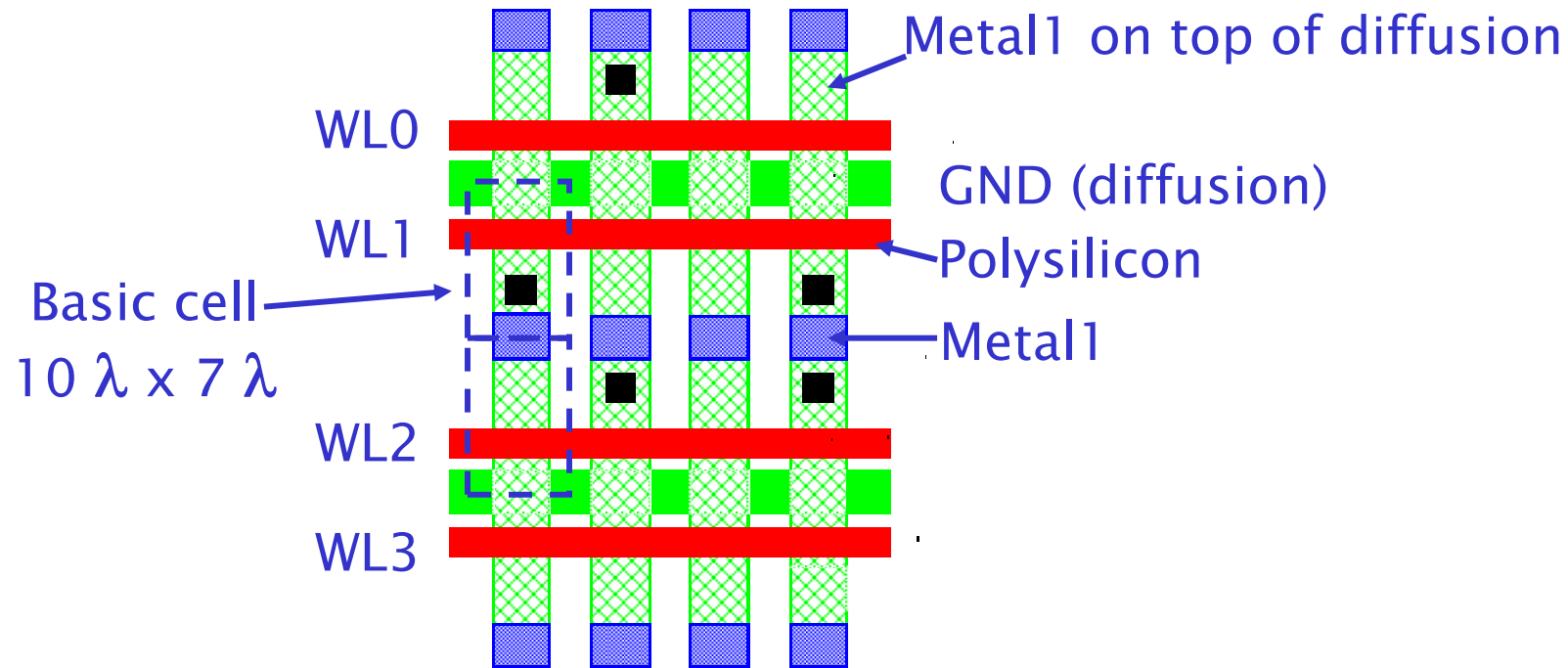


- Only 1 layer (metal-to-diffusion contact mask) is used to program memory array
- Programming of the memory can be delayed to one of last process steps

# ROM Cell: MOS NOR Alternative Layout

 

- Threshold raising implants disable transistors


# ROM Cell: MOS NAND

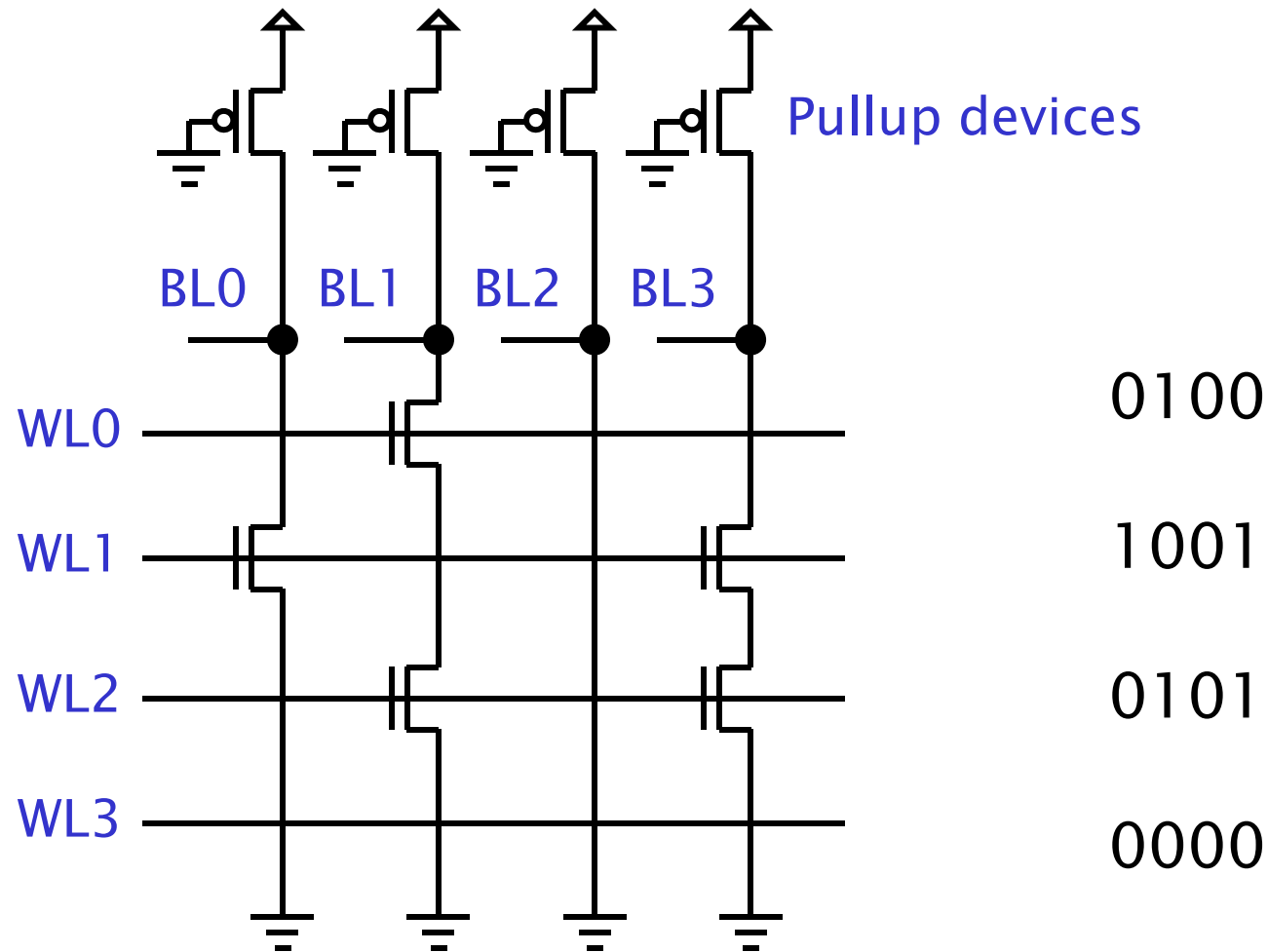

All word lines high by default with exception of selected row

[©Prentice Hall]

# ROM Cell: MOS NAND: Layout

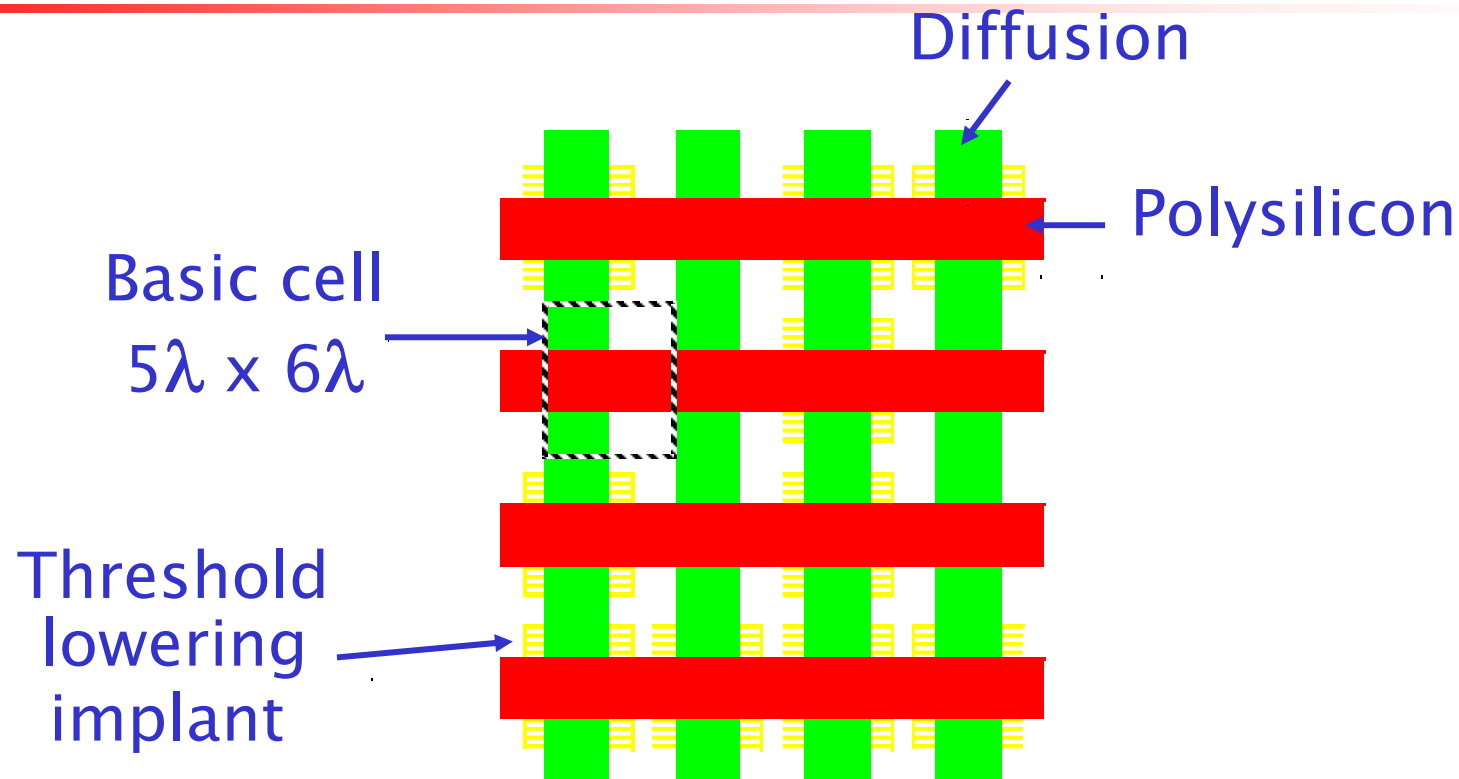

- No contact to Vdd or GND necessary  
→ drastically reduced cell size
- Loss in performance compared to NOR ROM
  - Why?

# ROM Cells: Summary

---

- Mask programmability
  - Precharged vs. pseudo-nMos
  - NAND cell, NOR cell
    - Area
    - Speed
  - Other types: EEPROM, etc.
-




# Outline

---

- Memory interface
  - Memory cells
    - Static memory cell
    - Dynamic memory cell
    - ROM cells
  - **Address decoders**
-

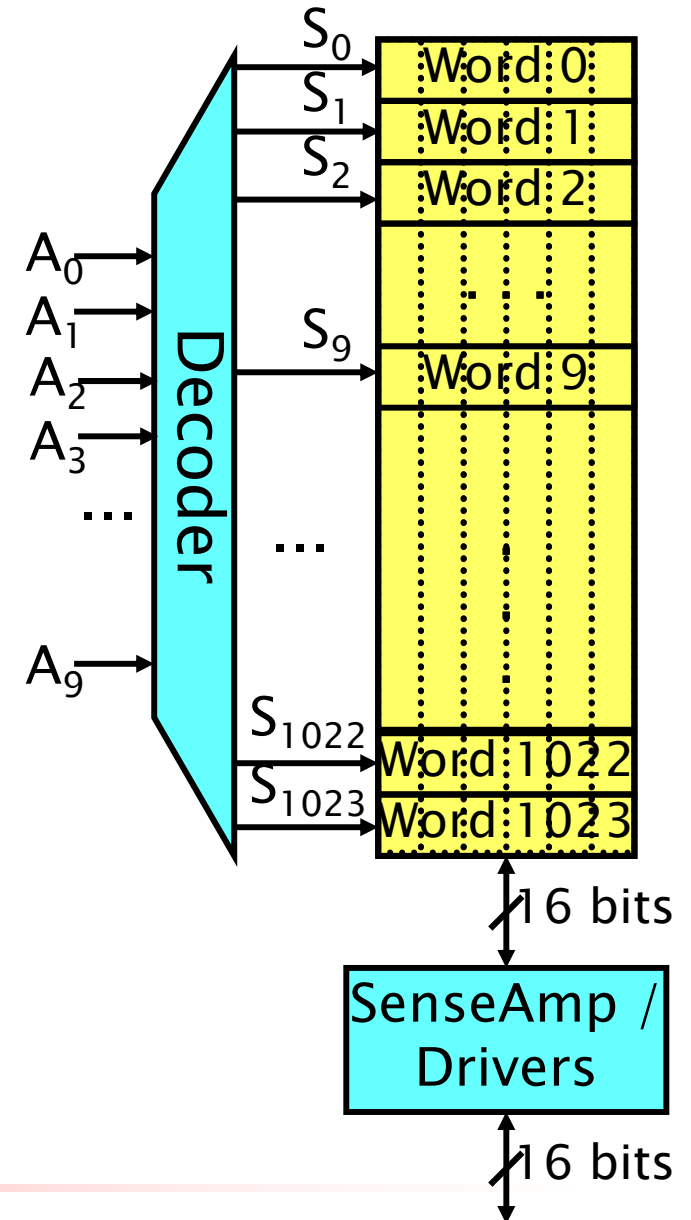
# Memory Cell Array Interface: Example

- Memory parameters:
  - 16-bit wide
  - 1024-word deep
- Accessing word 9
  - Address =  $0000001001_2$



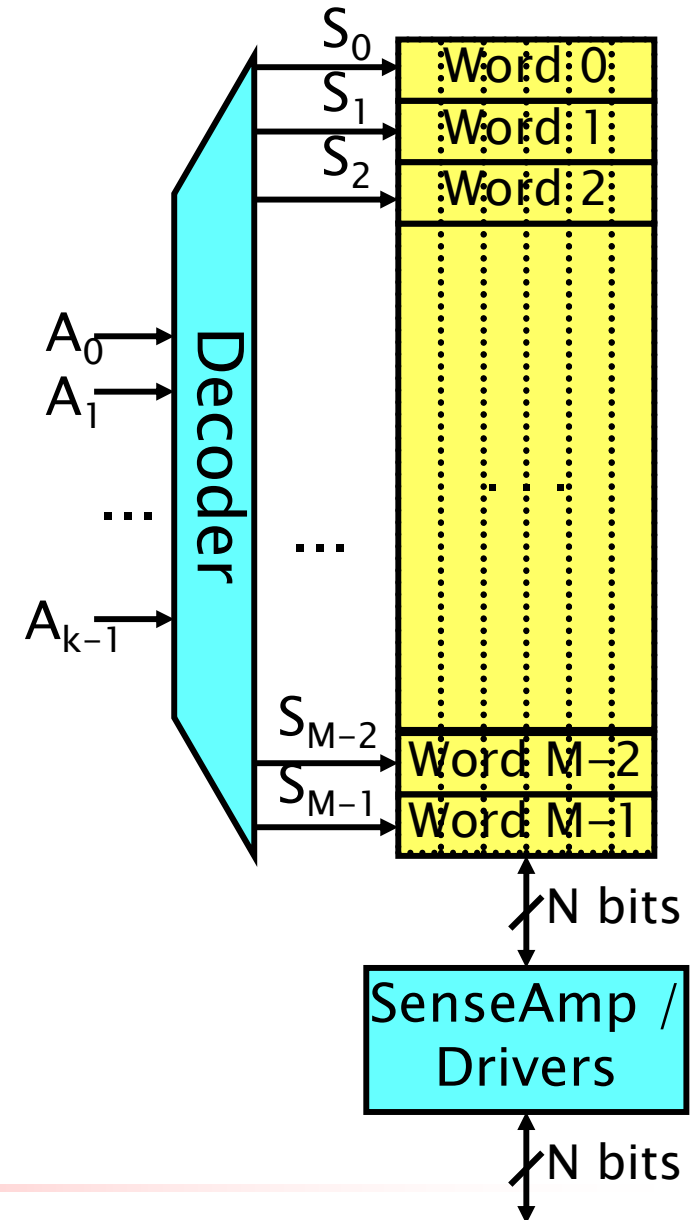
# Memory Cell Array Layout

- Memory performance (speed)
  - Storage cell speed (read, write)
  - Data bus capacitance
  - Periphery: address decoders, sense amplifiers, buffers
- Memory area
  - Cell array layout
- How to layout the cells array?
  - Linear is bad:
    - Long data busses → large capacity
    - A lot of cells connected to data bus
    - Decoder will have a lot of logic levels



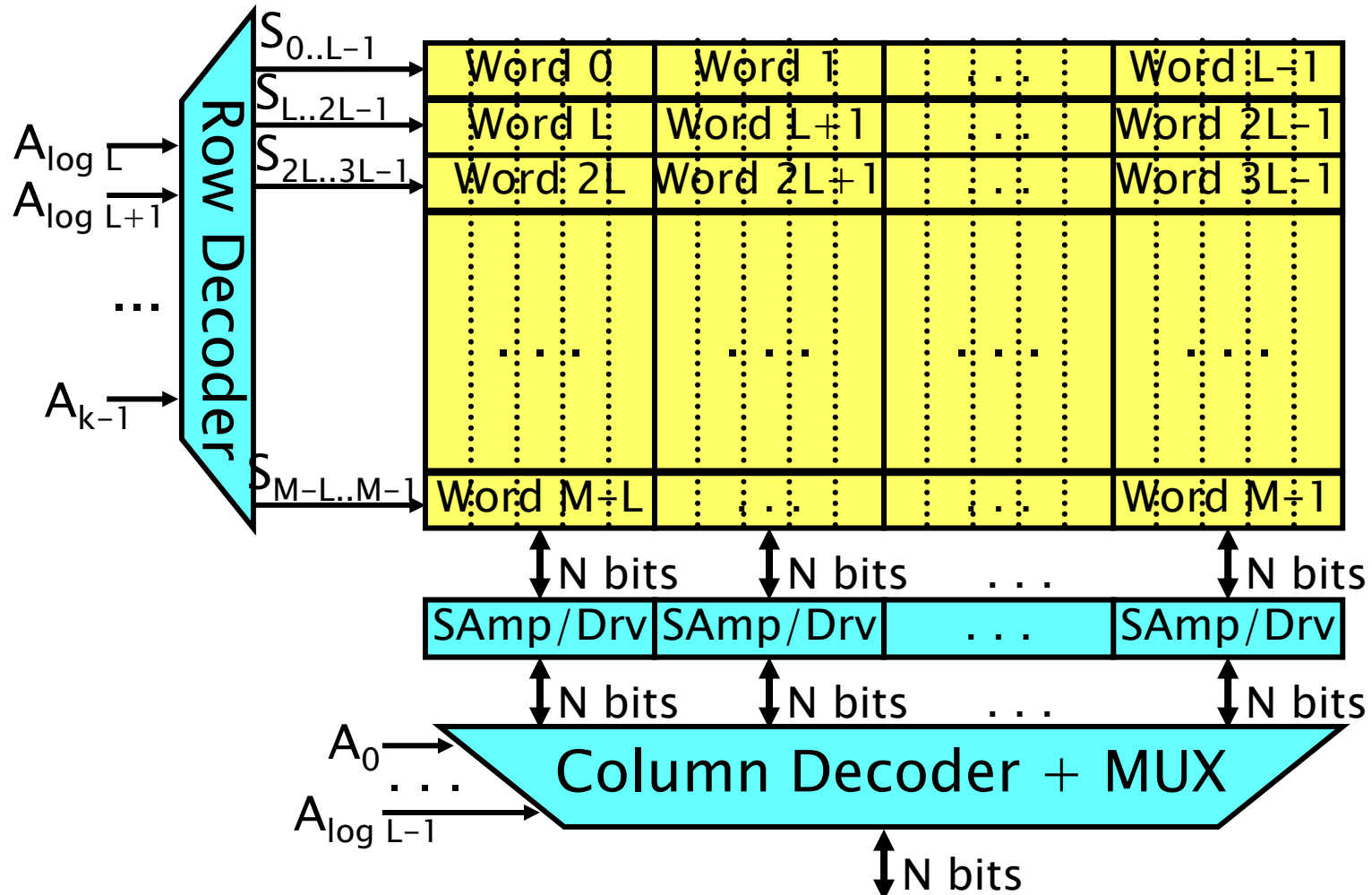
# Memory Cell Array Layout (cont.)

- Group the  $M$  words into  $M/L$  rows, each containing  $L$  words
- Benefits?



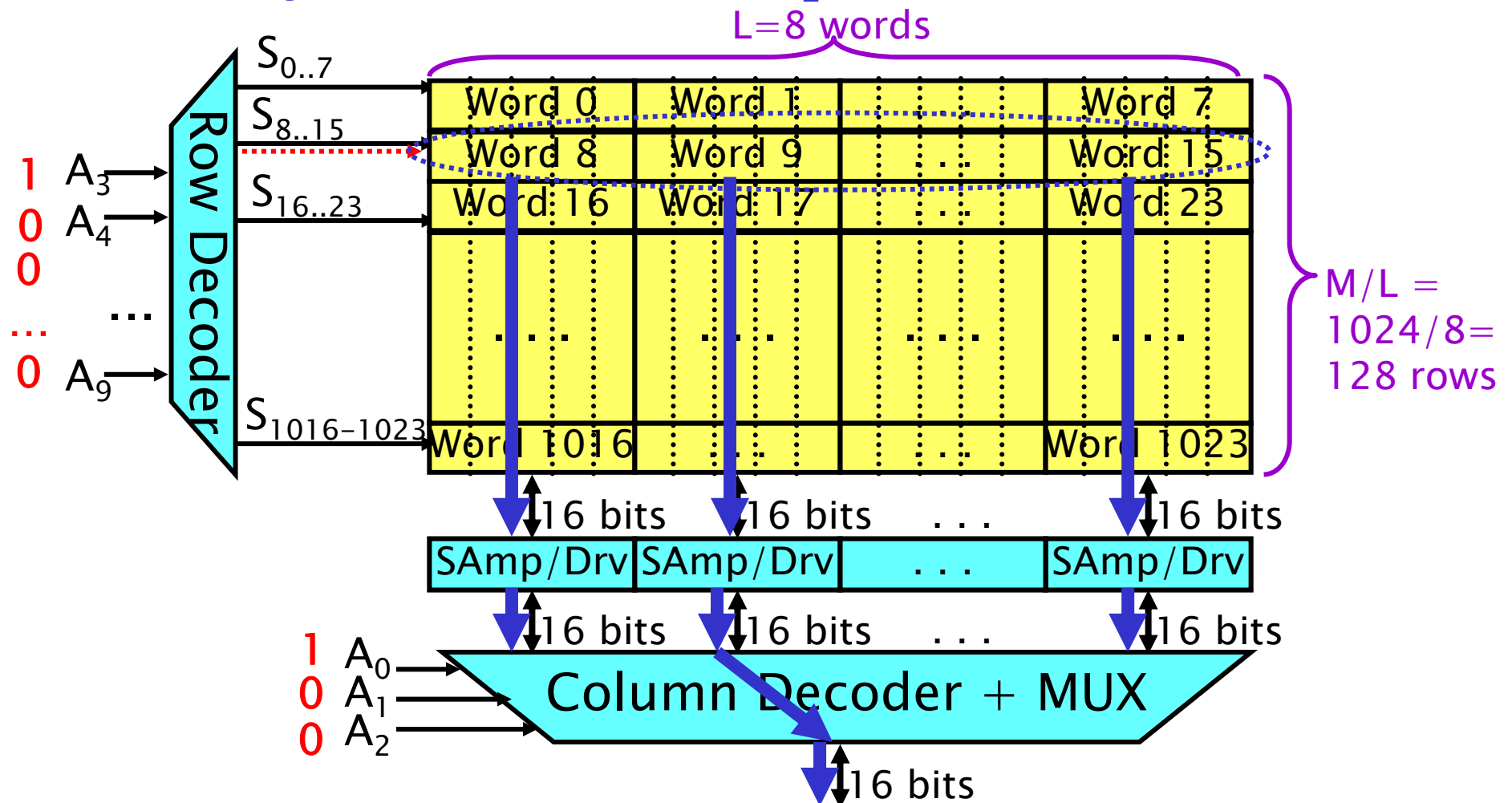
# Memory Cell Array Access Example

- word=16-bit wide(N), row=8 words(L), address=10 bits (k)
- Accessing word 9 =  $0000001001_2$



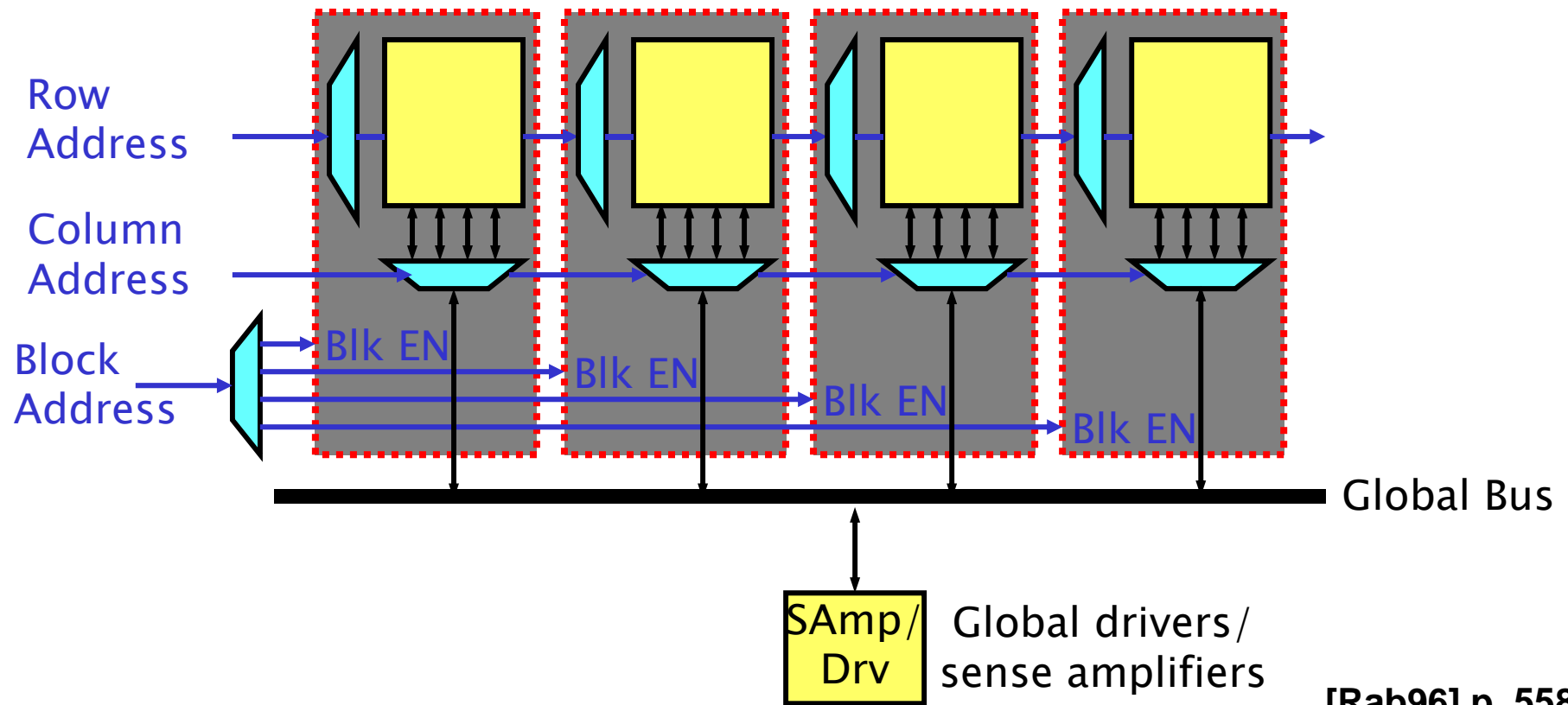
# Hierarchical Memory Structure

- Taking the idea one step further
  - Shorter wires within each block
  - Enable only one block addr decoder → power savings



 
# Decreasing Word Line Delay

- Word line delay comes into play!
  - We used to have long busses, made 2D array → shorter busses
  - But, longer word lines!
- How to decrease the delay on the word lines?
  - Break the word line by inserting buffers
  - Place the decoder in the middle




(a) Drive the word line from both sides

 

(b) Use metal bypass
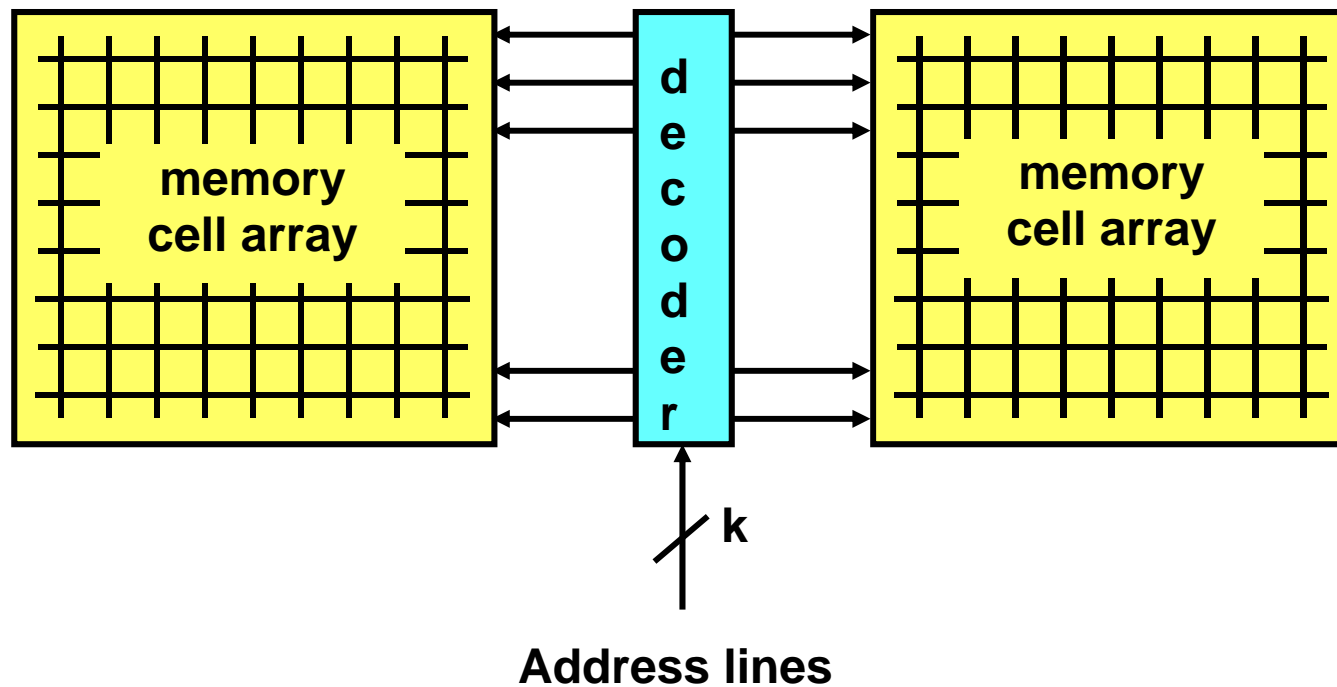
# Decreasing Word Line Delay (cont.)

- Place the decoder in the middle
- Add buffers to outputs of decoder





# Row Decoder Implementation

---

- Collection of  $2^k$  high fan-in ( $k$  inputs) logic gates
- Regular and dense structure
- N(AND) decoder

$$WL_0 = \overline{A_0} \cdot \overline{A_1} \cdot \overline{A_2} \cdot \overline{A_3} \cdot \overline{A_4} \cdot \overline{A_5} \cdot \overline{A_6} \cdot \overline{A_7} \cdot \overline{A_8} \cdot \overline{A_9}$$


$$WL_{511} = A_0 \cdot A_1 \cdot A_2 \cdot A_3 \cdot A_4 \cdot A_5 \cdot A_6 \cdot A_7 \cdot A_8 \cdot A_9$$

- NOR decoder


$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\overline{A_0} + \overline{A_1} + \overline{A_2} + \overline{A_3} + \overline{A_4} + \overline{A_5} + \overline{A_6} + \overline{A_7} + \overline{A_8} + \overline{A_9}}$$

# Row Decoder Implementation (cont.)

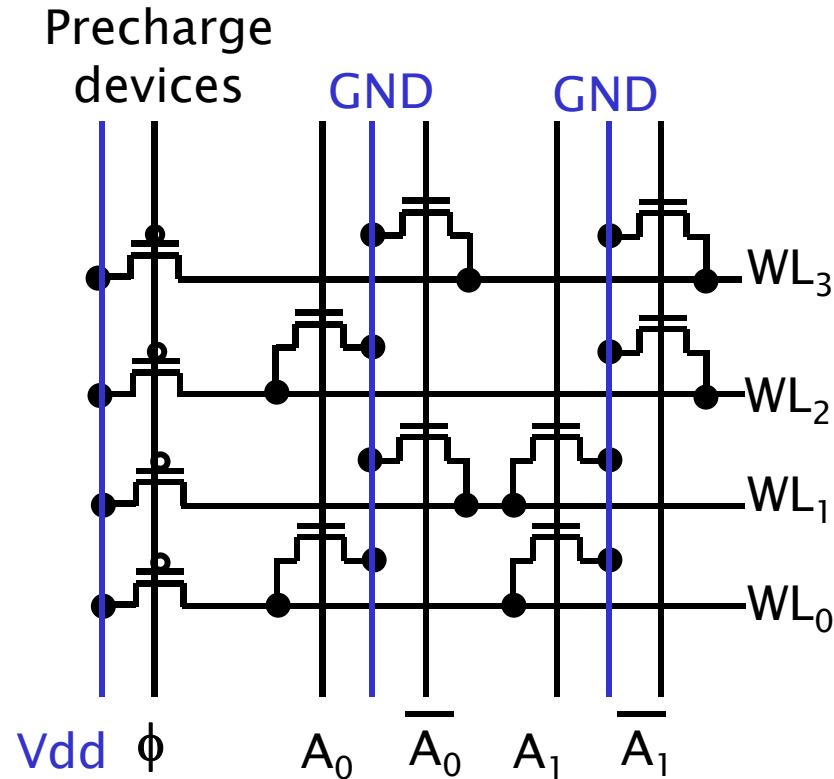


Dynamic 2-to-4 NOR Decoder

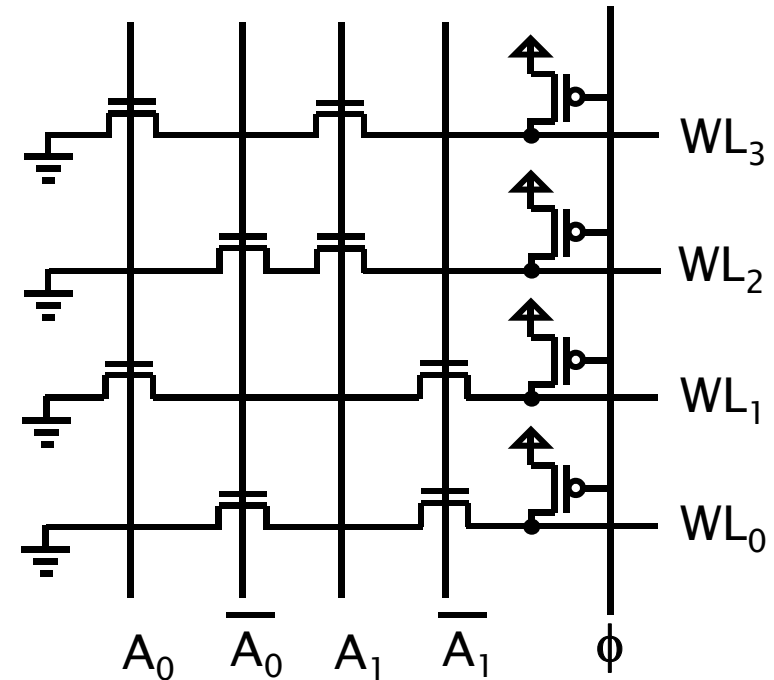

2-to-4 MOS Dynamic NAND Decoder


# Row Decoder Implementation (cont.)

 

Splitting decoder into two or more logic layers produces a faster and cheaper implementation

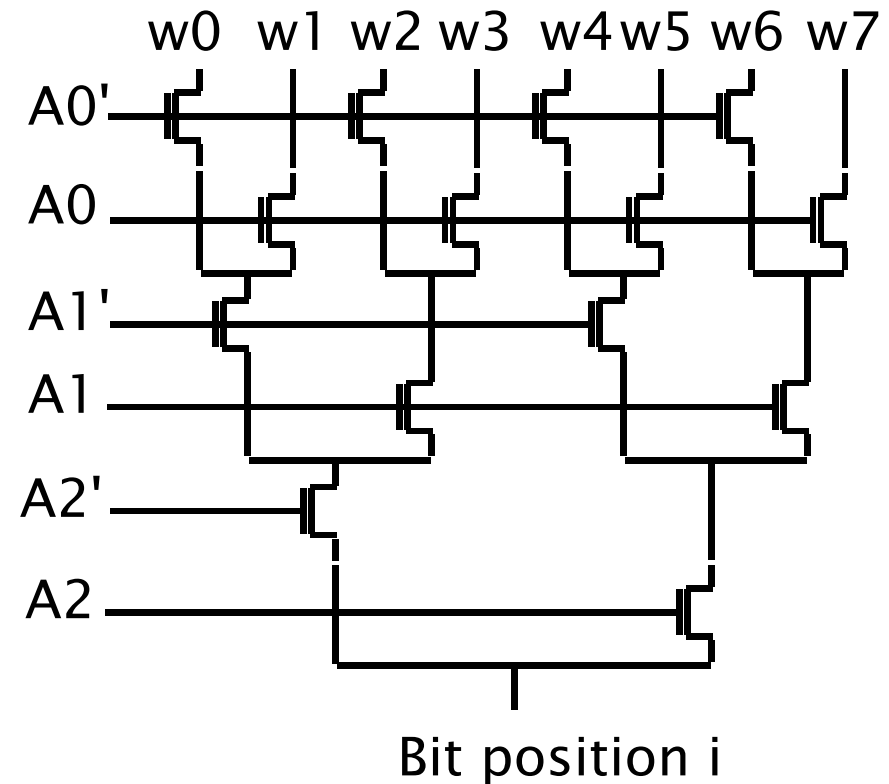
# Column Multiplexers: Tree-Based Decoder

- Route many inputs to a single output
  - Inputs come from different words, same bit position
- Series transistors are slow
  - On the critical path too
- Area?
  - One-bit very small, but have to repeat the “decoding” for all bit positions.


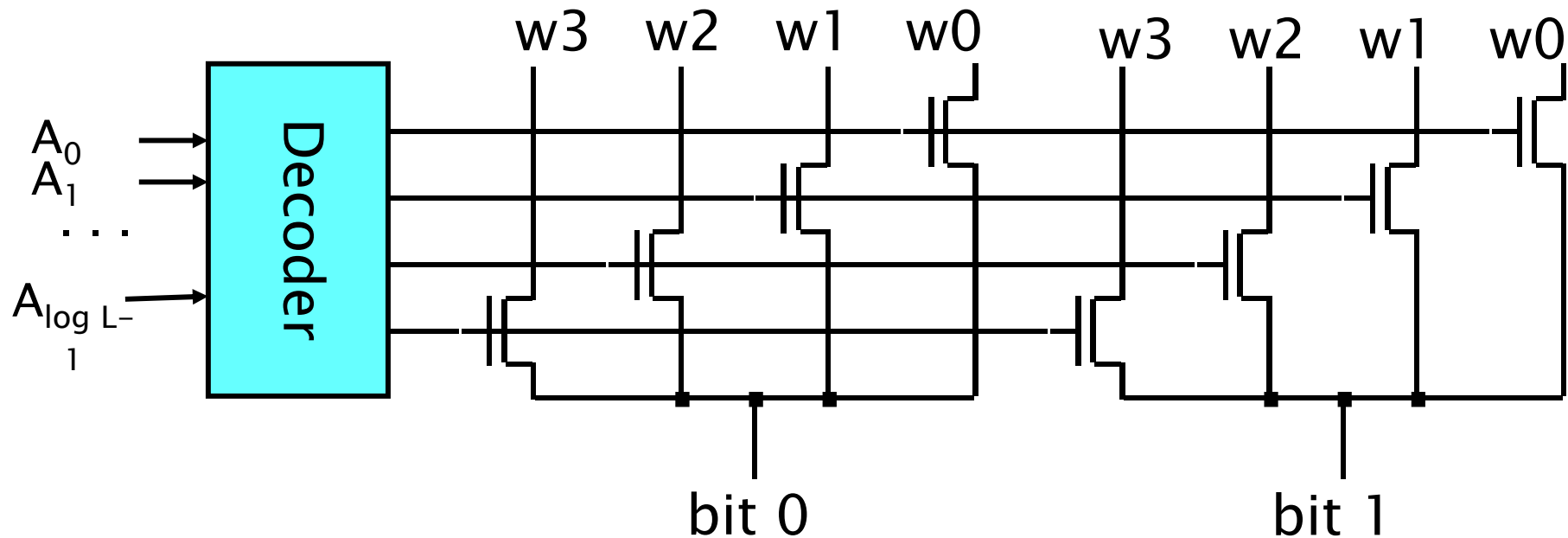
# Column Multiplexers: Faster Implementation

- Decode address into one-hot signals
- Each bit passes through single n-device or pass gate
- Column decoding done in parallel w/ row decoding




# Outline

---

- Memory interface
  - Memory cells
    - Static memory cell
    - Dynamic memory cell
    - ROM cells
  - Address decoders
  - **Content addressable memory (CAM)**
  - Non volatile memory cells
-

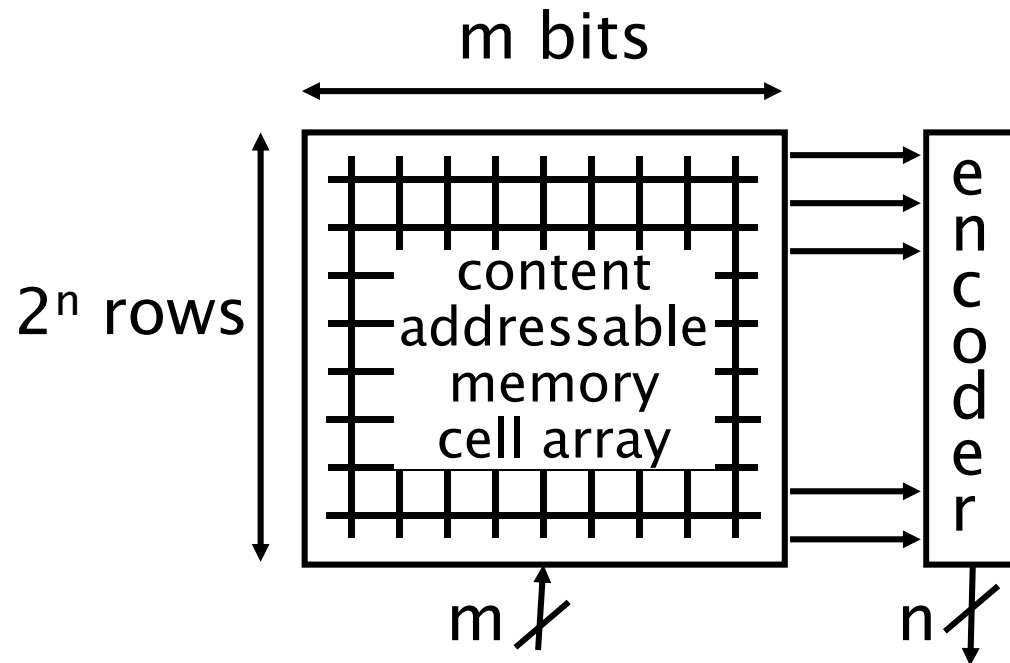
# Content Addressable Memory (CAM)

- Instead of address, provide data → find a match
  - Applications: cache, physical particle collider
- Needs “Encoder”:
  - Inverse function of decoder
  - Take a one-hot collection of signals and encode them



 
# Content Addressable Memory Cell

- Read and write like normal 6T memory cell
- Match signal is precharged to 1, pulled to 0 if no match
  - Send data on bit' and data' on bit for matching
  - Match remains 1 iff all bits in word match






# Encoders

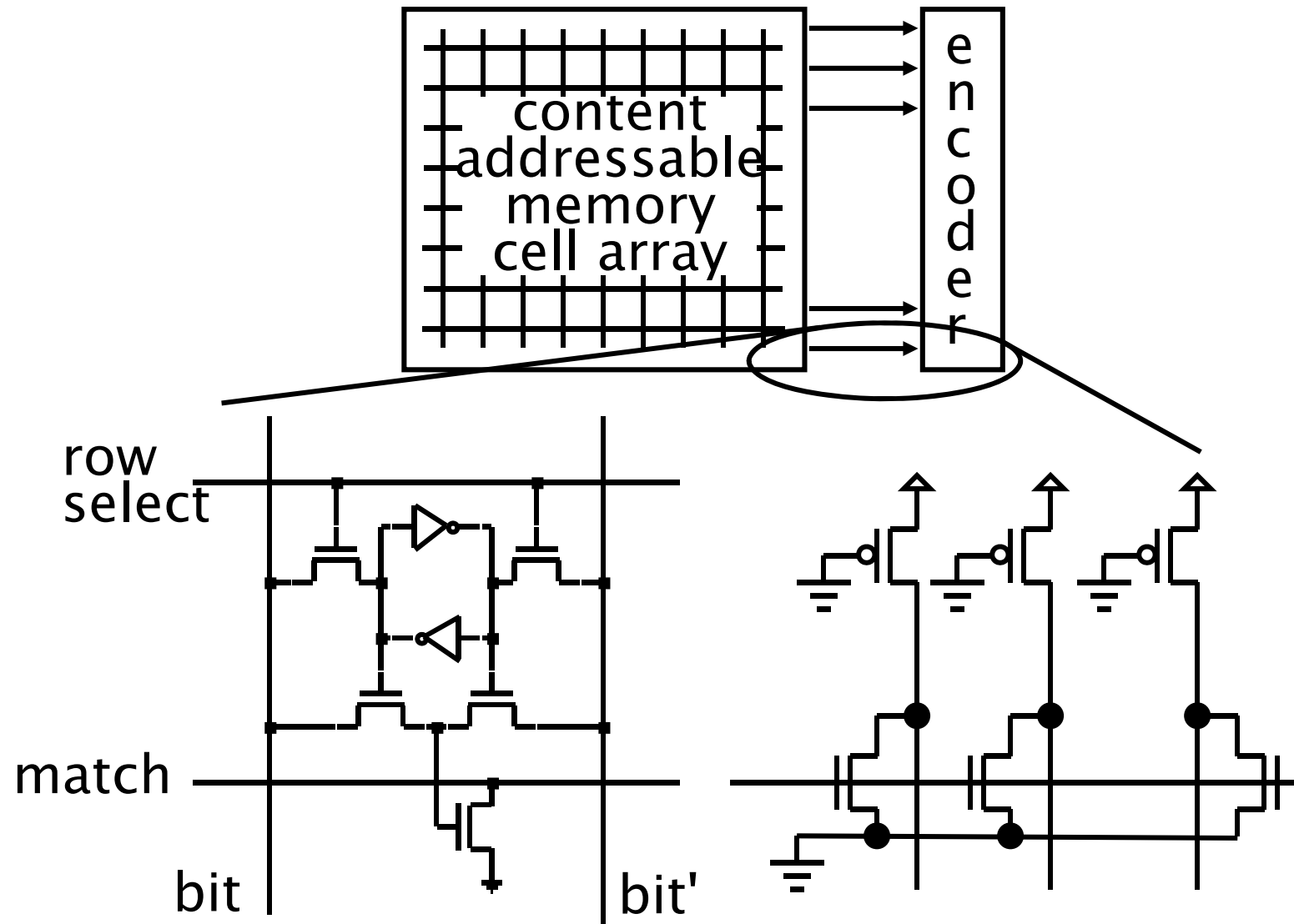
 
# Content Addressable Memory (CAM)

---

- Writing is done as normal SRAM
  - Address decoder needed
  - Drive row select
- $\frac{1}{2} n \log n$  transistors on the address lines (in encoder)



# Outline

---


- Registers (flip-flops), shift registers
  - Memory interface
  - Memory cells
    - Static memory cell
    - Dynamic memory cell
    - ROM cells
  - Address decoders
  - Content addressable memory (CAM)
  - **Non volatile memory cells**
-

# Non-Volatile Memory Cells


---

- Programmable after fabrication
  - Keep their configuration even after the supply voltage is disconnected
  - Basic idea:
    - Use a floating strip of polysilicon between the substrate and the gate
    - Put charges on the floating gate
    - Increase threshold voltage → disable the device
  - Different types based on the erasure method
-

# Floating-Gate Transistor (FAMOS)

 


(a) Device cross-section

 


(b) Schematic symbol


# Floating-Gate Transistor: Programming

 

Avalanche injection.

 


 Removing programming voltage leaves charges trapped




Programming results in higher  $V_T$


# FLOTOX EEPROM

 

(a) Flotox transistor

 


(b) Fowler-Nordheim I-V characteristics

 

(c) EEPROM cell during a read operation


# FLASH EEPROM

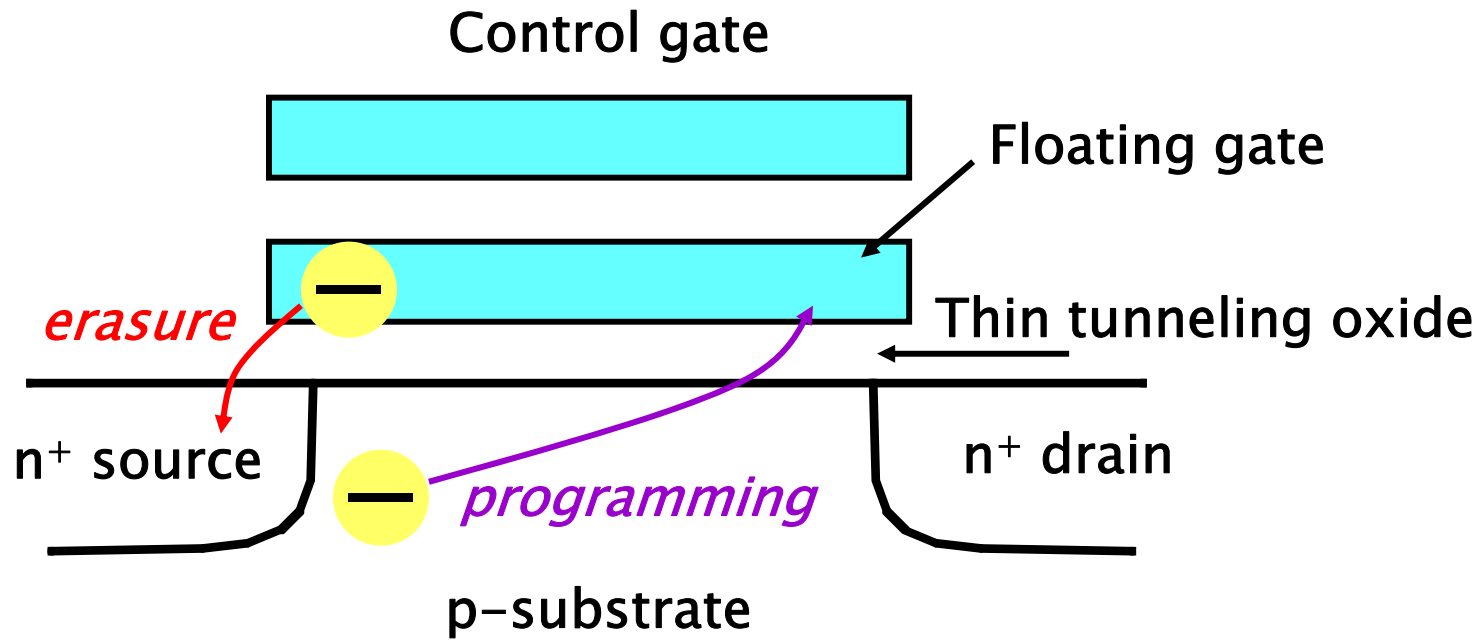



# Cross-Section of NVM Cells

---

 

Courtesy Intel

# Characteristics of Some NVM Cells

---

	EPROM [Tomita91]	EEPROM [Terada89, Pashley89]	Flash EEPROM [Jinbo92]
Memory size	16 Mbit (0.6 $\mu\text{m}$ )	1 Mbit (0.8 $\mu\text{m}$ )	16 Mbit (0.6 $\mu\text{m}$ )
Chip size	7.18 x 17.39 $\text{mm}^2$	11.8 x 7.7 $\text{mm}^2$	6.3 x 18.5 $\text{mm}^2$
Cell size	3.8 $\mu\text{m}^2$	30 $\mu\text{m}^2$	3.4 $\mu\text{m}^2$
Access time	62 nsec	120 nsec	58 nsec
Erasure time	minutes	N.A.	4 sec
Programming time/word	5 $\mu\text{sec}$	8 msec/word, 4 sec /chip	5 $\mu\text{sec}$
Erase/Write cycles [Pashley89]	100	$10^5$	$10^3$ - $10^5$

---